

19CSE19281

DIGITAL CIRCUITS AND SYSTEMS


LAB PROJECT

GROUP - J

S Abhishek - AM.EN.U4CSE19147
Rahan Manoj - AM.EN.U4CSE19144
Harsha Sathish - AM.EN.U4CSE19123
Arvind Kumar - AM.EN.U4CSE19109
Rohit Menon - AM.EN.U4CSE19146

**DESIGN A MEALY FSM DETECTOR FOR THE
SEQUENCE 111101 AND IMPLEMENT USING
TINKER CAD**

STATE DIAGRAM

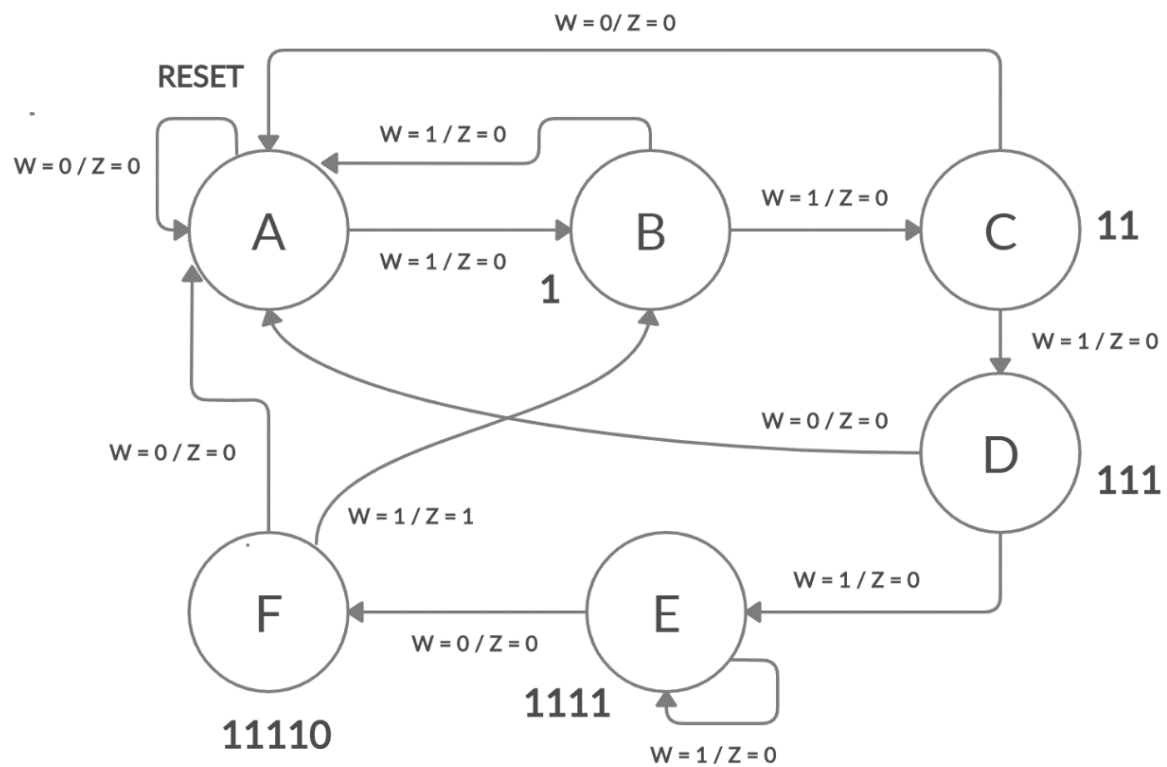

STATE TABLE

	NEXT STATE		OUTPUT	
	W = 0	W = 1	W = 0	W = 1
A	A	B	0	0
B	A	C	0	0
C	A	D	0	0
D	A	E	0	0
E	F	E	0	0
F	A	B	0	1

STATE ASSIGNED TABLE

	PRESENT STATE			NEXT STATE						OUTPUT	
				W = 0			W = 1			W = 0	W = 1
	Y3	Y2	Y1	Y3	Y2	Y1	Y3	Y2	Y1	Z	Z
A	0	0	0	0	0	0	0	0	1	0	0
B	0	0	1	0	0	0	0	1	0	0	0
C	0	1	0	0	0	0	0	1	1	0	0
D	0	1	1	0	0	0	1	0	0	0	0
E	1	0	0	1	0	1	1	0	0	0	0
F	1	0	1	0	0	0	0	0	1	0	1

KMAP FOR Y1

		y2 y1			
		00	01	11	10
w y3	00	0	0	0	0
	01	1	0	D	D
	11	0	1	D	D
	10	1	0	0	1

$$Y1 = w' y3 y1' + y1 w y3 + y1' w y3'$$

KMAP FOR Y2

		y2 y1			
		00	01	11	10
w y3	00	0	0	0	0
	01	0	0	D	D
	11	0	0	D	D
	10	0	1	0	1

$$Y2 = y1 y2' y3' w + w y2 y1'$$

KMAP FOR Y3

		y2 y1			
		00	01	11	10
w y3	00	0	0	0	0
	01	1	0	D	D
	11	1	0	D	D
	10	0	0	1	0


$$Y3 = y1' y3 + w y1 y2$$

KMAP FOR Z



$y_2 y_1$ $w y_3$					
		00	01	11	10
00	0	0	0	0	0
01	0	0	0	D	D
11	0	1	D	D	D
10	0	0	0	0	0

$$Z = w y_3 y_1$$

CIRCUIT

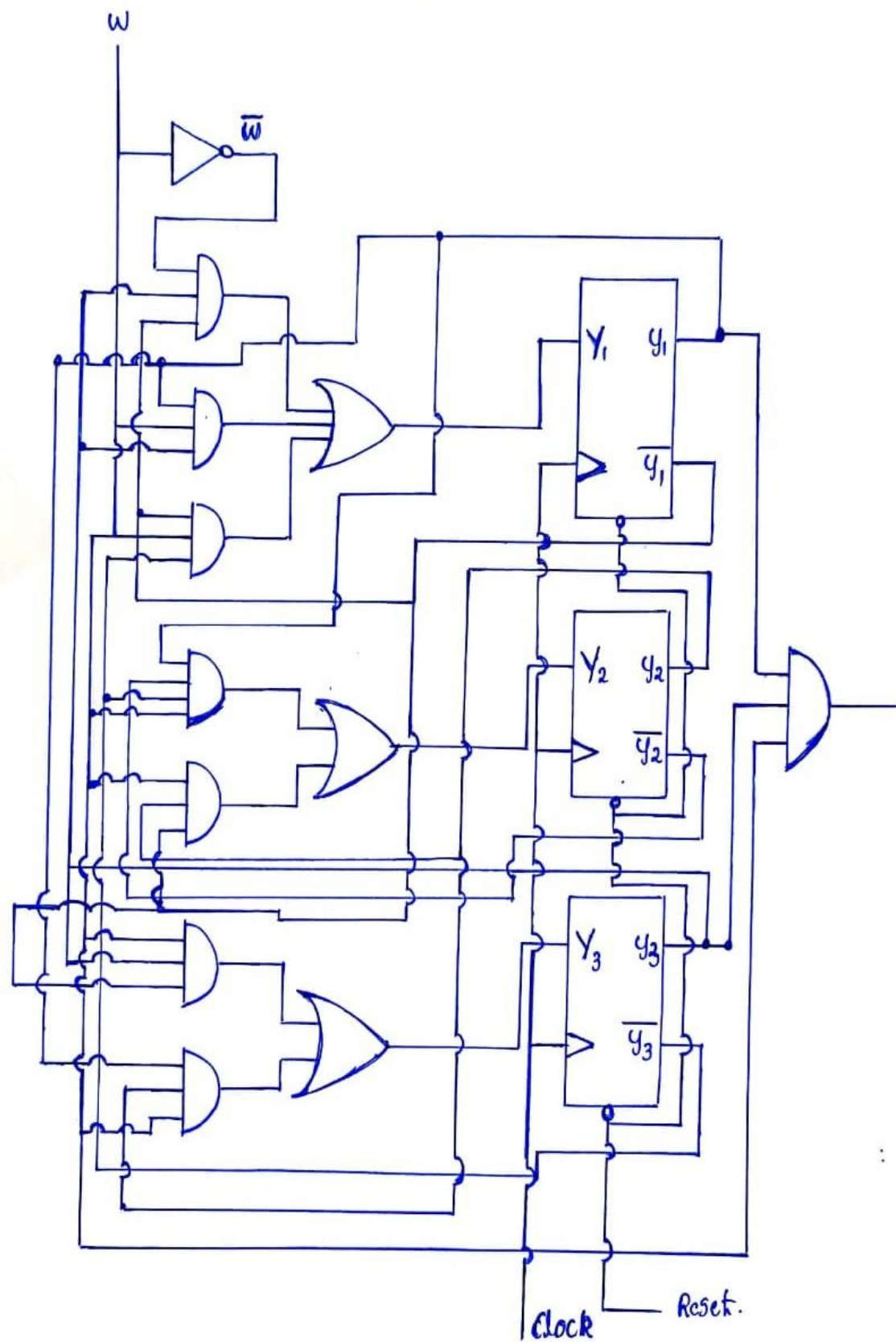

TINKER CAD IMPLEMENTATION

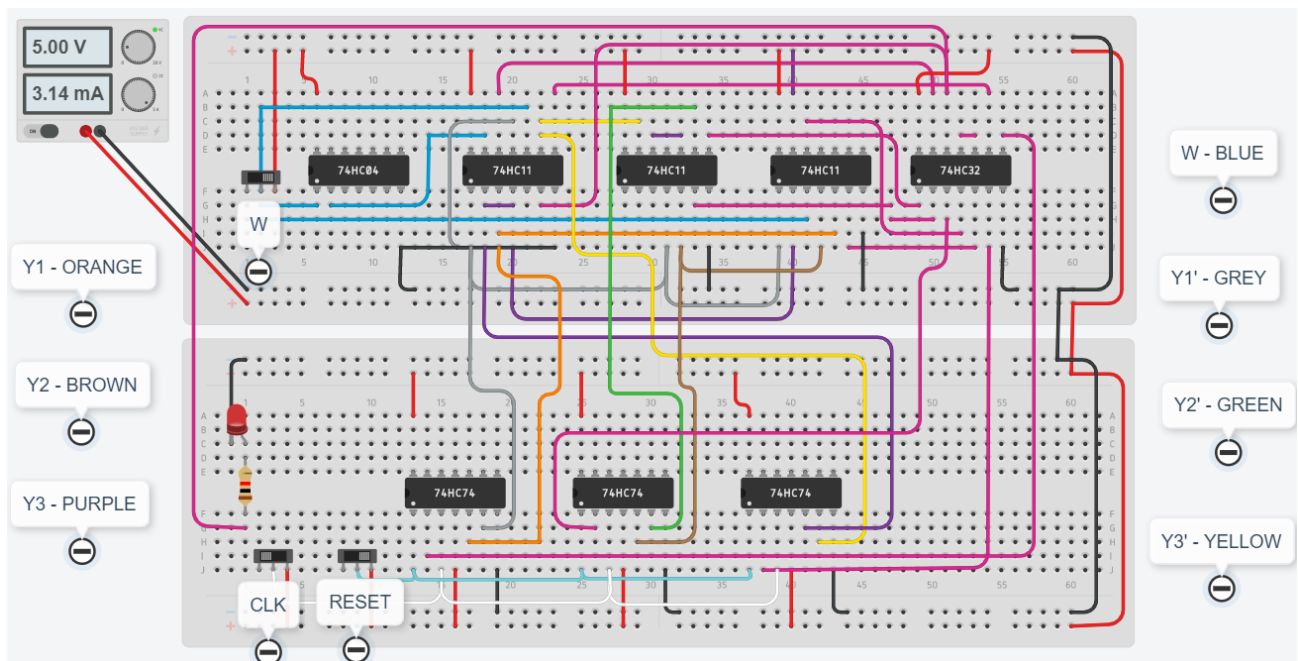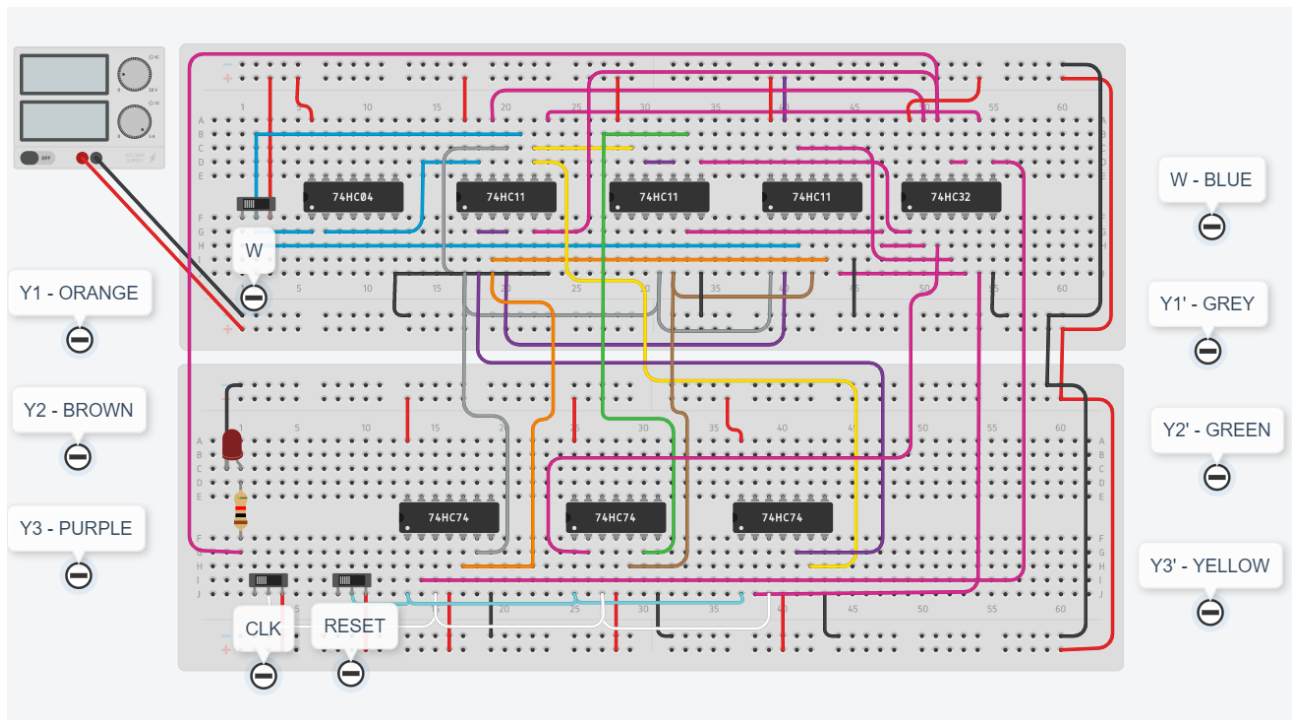

RESULT

- The logic circuit was implemented in accordance with the theory and output was obtained successfully by the glow of LED.